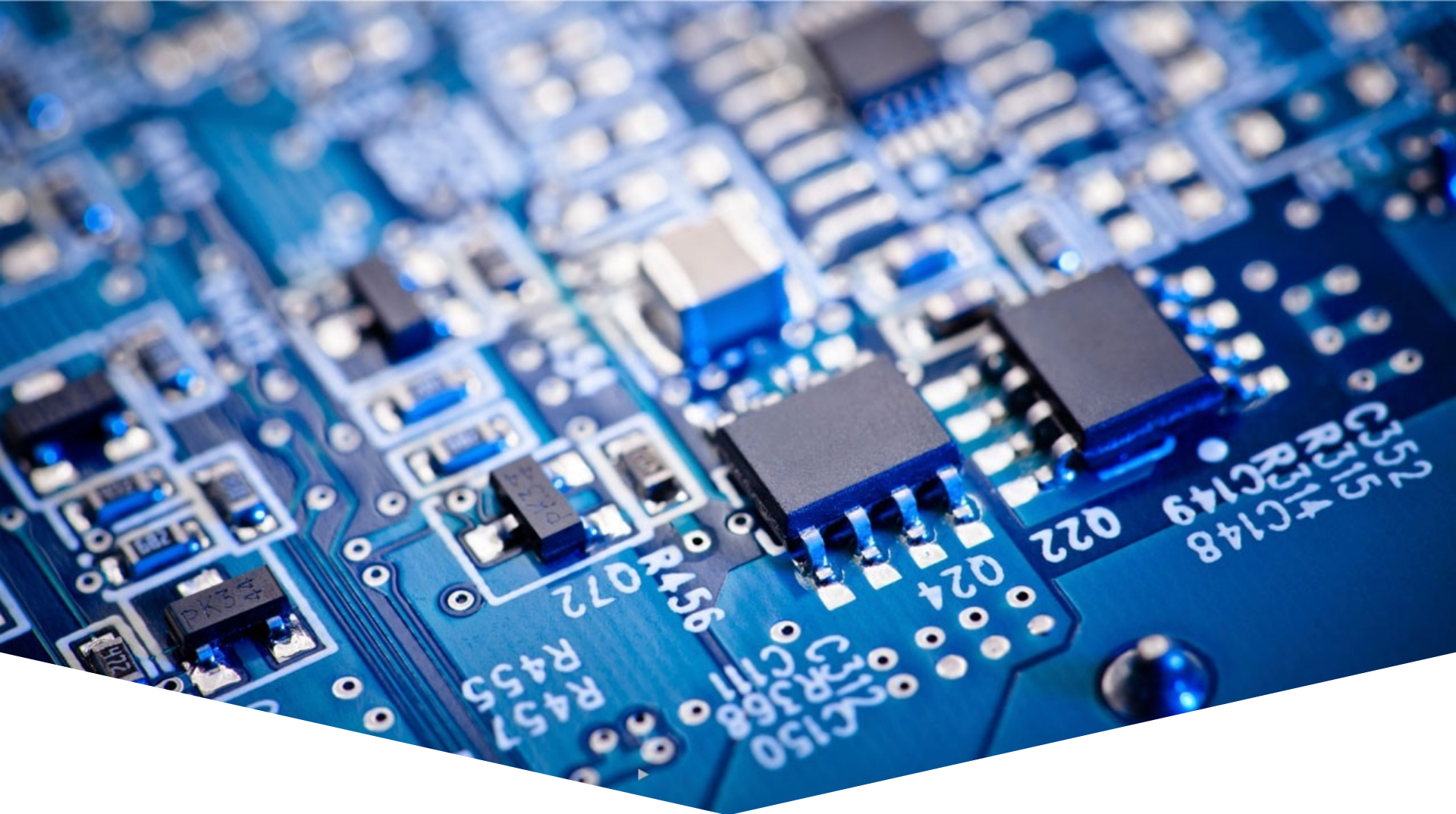




ANALOGUE ELEKTRONICA 2

CLASS-D AMPLIFIERS

overtref jezelf



Overzicht

- Power Amplifiers
 - Power Transistors
 - Heat Sinks
- Classes of Amplifiers
 - Class A
 - Class AB
 - Class D
- Class D amplifier
 - RLC-Filter
 - Bootstrap Circuit Design

Power Amplifiers



■ Power Amplifiers:

- Deliver large amounts of power ($> 100 \text{ W}$) to a passive load
- Typically built with BJT-transistor or MOSFETs

■ Total harmonic distortion (THD):

- RMS value of harmonic components of the output signal
- Fundamental frequency excluded
- Expressed as a percentage of the fundamental

Power Transistors

■ Physical Transistor Limitations:

- Maximum rated current: typically I_C or I_{DS}
- Maximum rated voltage: typically U_{CE} or U_{DS}
- Maximum rated power: $P = U_{CE} \cdot I_C$ or $P = U_{DS} \cdot I_{DS}$

■ Types of transistor: BJT and MOSFET

■ Also to consider:

- Maximum allowed temperature: function of rate at which heat is removed

■ Example: MJ15003 (NPN) and MJ15004 (PNP)

- $U_{CE,max} = 140 \text{ V}$, $P_{diss} = 250 \text{ W}$, $I_{C,DC} = 20 \text{ A}$, TO-3 case



Power BJT Transistor

Table 8.1

Comparison of the characteristics and maximum ratings of a small-signal and power BJT

Parameter	Small-Signal BJT (2N2222A)	Power BJT (2N3055)	Power BJT (2N6078)
$V_{CE}(\text{max})$ (V)	40	60	250
$I_C(\text{max})$ (A)	0.8	15	7
$P_D(\text{max})$ (W) (at $T = 25^\circ\text{C}$)	1.2	115	45
β	35–100	5–20	12–70
f_T (MHz)	300	0.8	1

- **DC current gain is not a constant:**
 - Drops at higher current
 - Much lower than a small-signal transistor
- **Watch the breakdown voltage mechanism:**

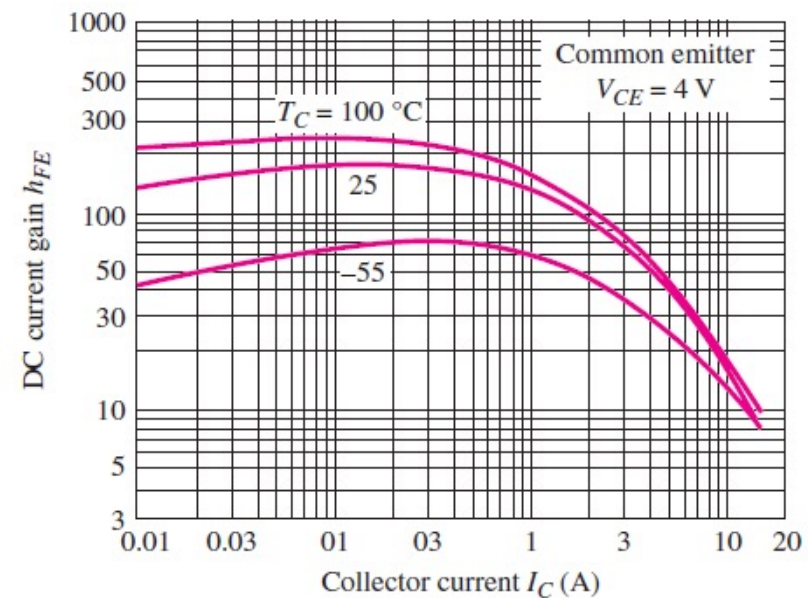
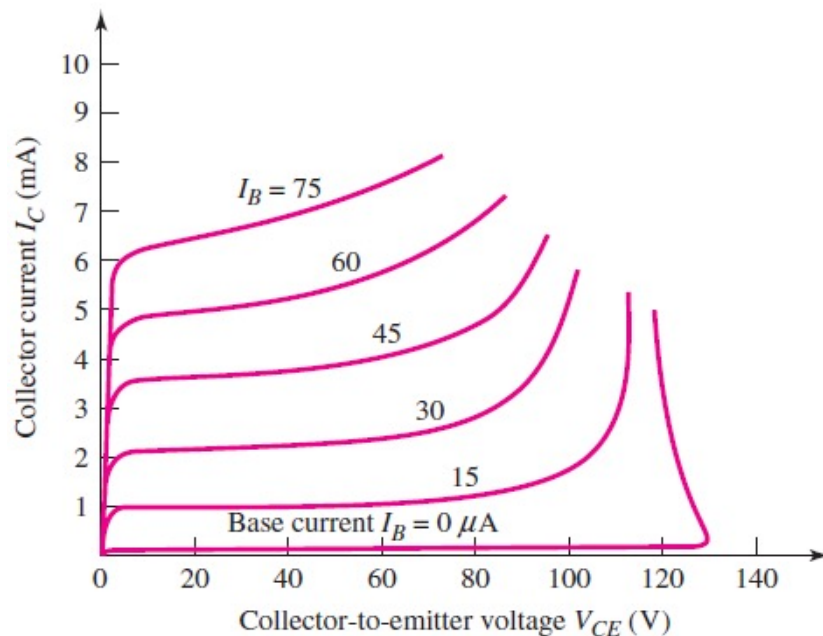


Figure 8.1 Typical dc beta characteristics (h_{FE} versus I_C) for 2N3055

Safe Operating Area (SOA)

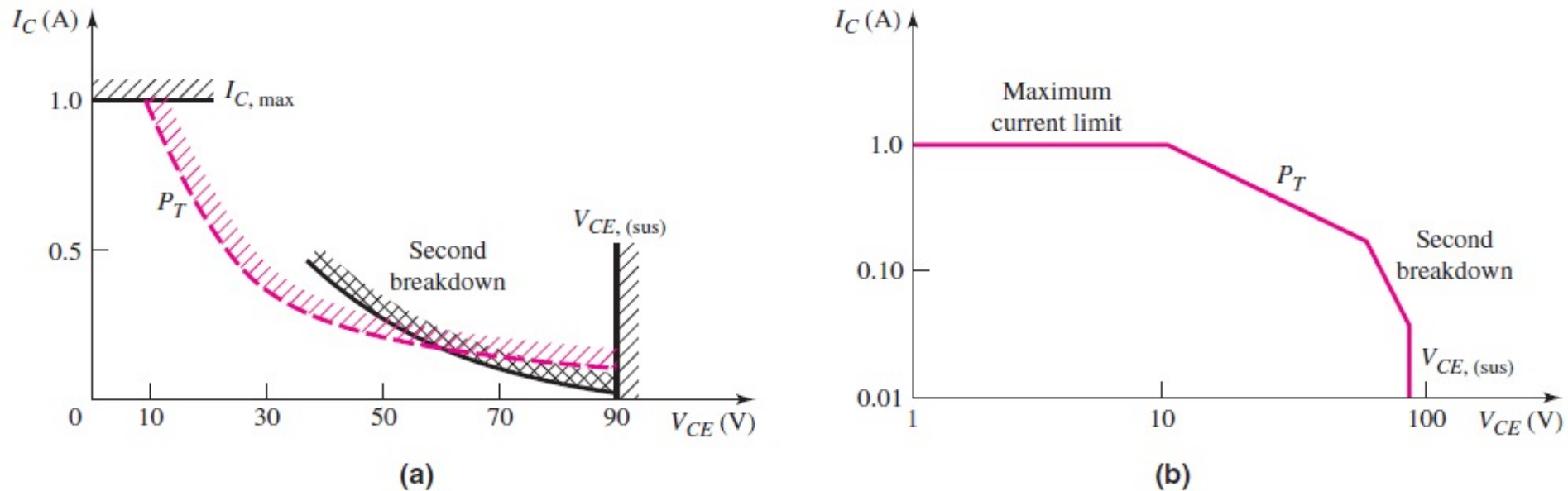


Figure 8.3 The safe operating area of a bipolar transistor plotted on: (a) linear scales and (b) logarithmic scales

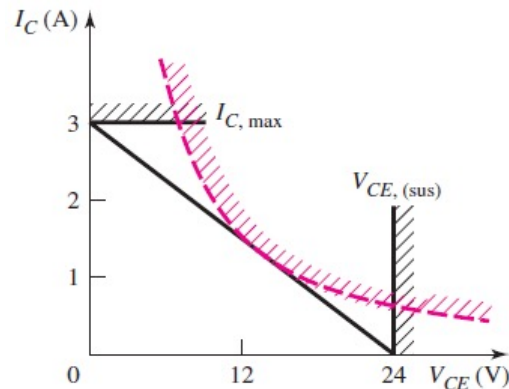


Figure 8.5 DC load line within the safe operating area


Power MOSFETs

Table 8.2 Characteristics of two power MOSFETs


Parameter	2N6757	2N6792
$V_{DS}(\text{max})$ (V)	150	400
$I_D(\text{max})$ (at $T = 25^\circ\text{C}$)	8	2
P_D (W)	75	20

No thermal runaway

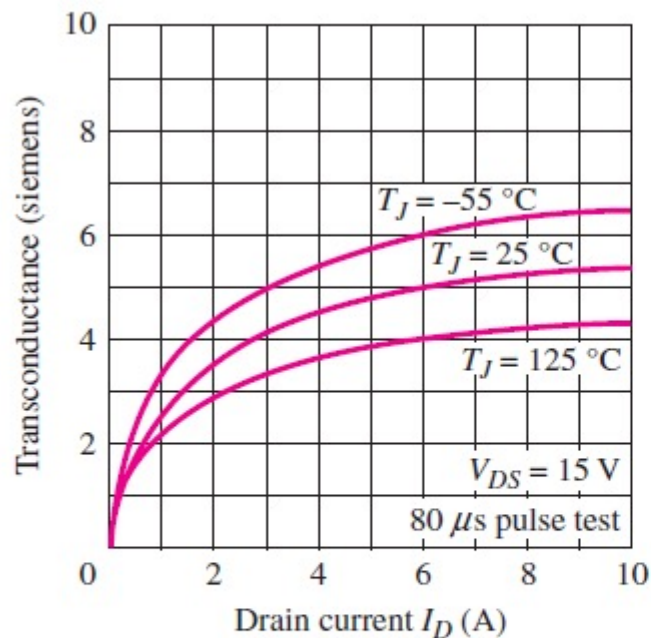- Transconductance decreases with temperature



(a)

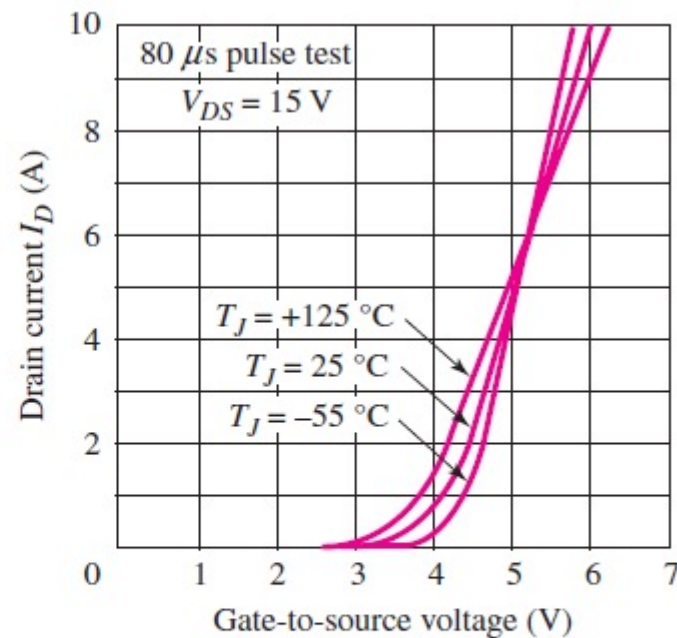

(b)

Figure 8.7 Typical characteristics for high-power MOSFETs: (a) transconductance versus drain current; (b) transfer characteristics

Power MOSFETs

Structure of MOSFETs

- HEXFET:
 - N-channel: IRF540
 - P-channel: IRF9540
- Normal FET:
 - N-channel: IRF530
 - P-channel: IRF9530

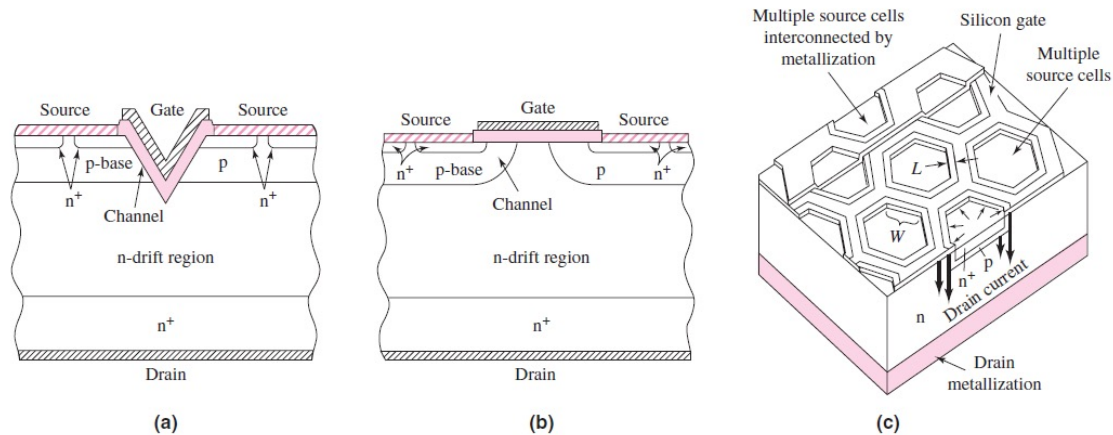
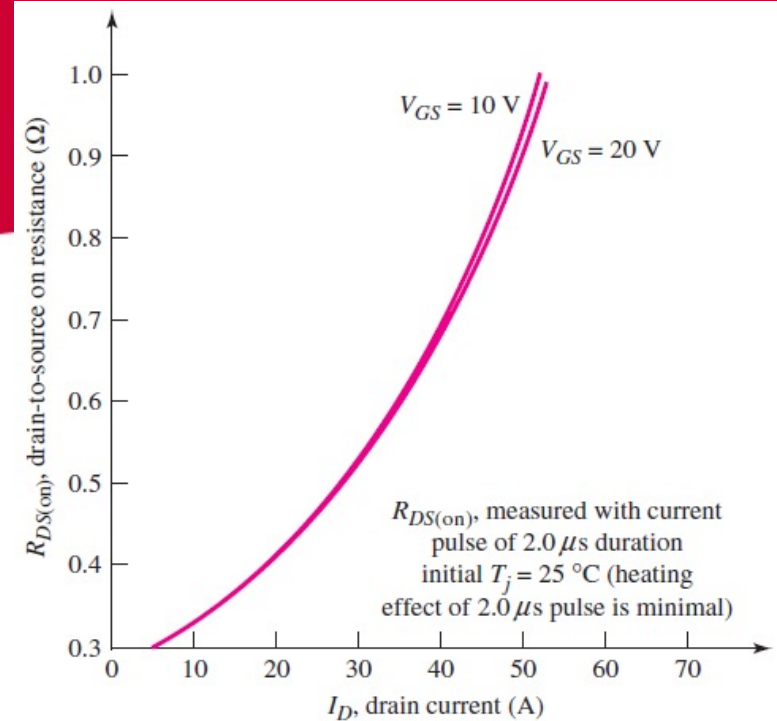


Figure 8.8 (a) Cross section of a VMOS device; (b) cross section of DMOS device; (c) HEXFET structure

Heatsinks

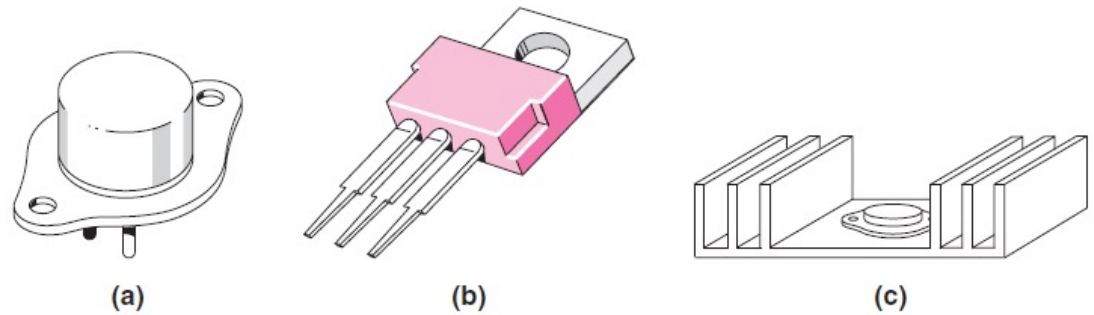


Figure 8.10 Two packaging schemes: (a) and (b) for power transistors and (c) typical heat sink

Max. Temp. Transistor (Silicium)

■ 150 °C – 200 °C

Heatsink needed!

■ What heatsink?

■ Θ [°C/W]: smaller = larger heatsink



Thermodynamics Law:

■ Comparable to Ohm's law

■ ΔT : Temperature difference [°C]

■ P_j : Power dissipation [W]

■ Θ : Thermal Resistance [°C/W]

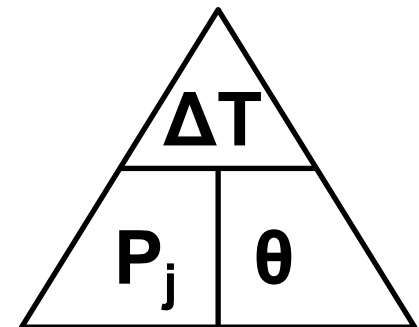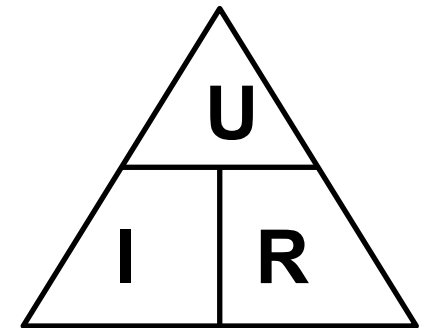

Heatsink calculation

Example:


- Transistor Power Rating: 2 W
- Thermal Resistance Junction -> Case: 5 °C/W
- Thermal Resistance Case -> Heatsink: 2 °C/W
- Thermal Resistance Heatsink -> Ambient: 10 °C/W

Hoe groot zijn de temperaturen?

- What heatsink?
- $T_a = 25\text{ °C}$ (omgevingstemperatuur)

Thermodynamica wet:

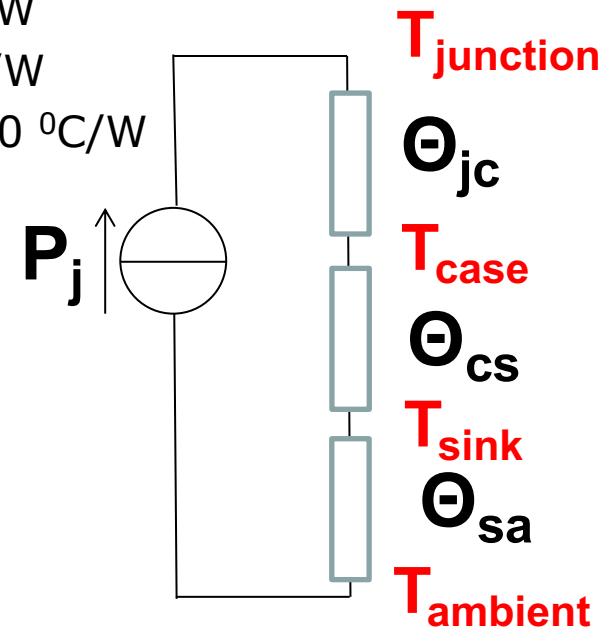- Vergelijkbaar met wet van Ohm
- ΔT : Temperatuurverschil [°C]
- P_j : Power dissipation [W]
- Θ : Thermal Resistance [°C/W]



Heatsink calculation

Example:

- Transistor Power Rating: 2 W
- Thermal Resistance Junction -> Case: 5 °C/W
- Thermal Resistance Case -> Heatsink: 2 °C/W
- Thermal Resistance Heatsink -> Ambient: 10 °C/W

Solution:

$$\Delta T_{\text{sink,ambient}} = T_{\text{sink}} - T_{\text{ambient}} = 2 \times 10 = 20 \text{ }^{\circ}\text{C}$$


$$T_{\text{ambient}} = 25 \text{ }^{\circ}\text{C} \Rightarrow T_{\text{sink}} = 45 \text{ }^{\circ}\text{C}$$

$$\Delta T_{\text{case,ambient}} = T_{\text{case}} - T_{\text{ambient}} = 2 \times (10+2) = 24 \text{ }^{\circ}\text{C}$$

$$T_{\text{ambient}} = 25 \text{ }^{\circ}\text{C} \Rightarrow T_{\text{case}} = 49 \text{ }^{\circ}\text{C}$$

$$\Delta T_{\text{junction,ambient}} = T_j - T_a = 2 \times (10+2+5) = 34 \text{ }^{\circ}\text{C}$$
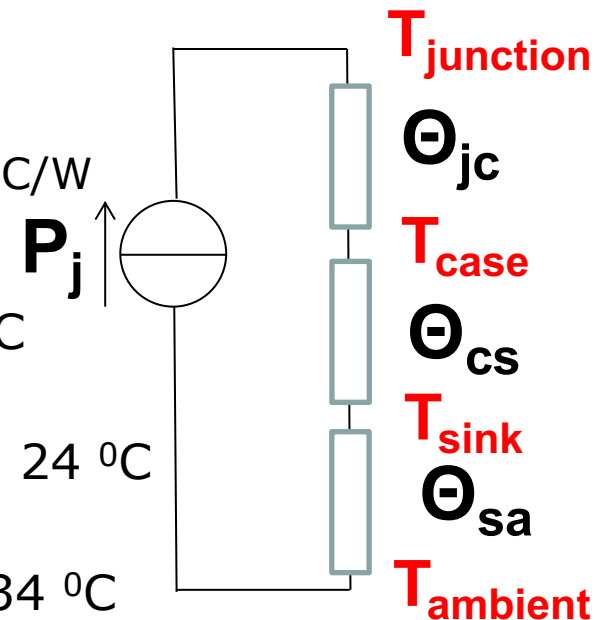
$$T_{\text{ambient}} = 25 \text{ }^{\circ}\text{C} \Rightarrow T_{\text{junction}} = 59 \text{ }^{\circ}\text{C}$$



Heatsink calculation


Example MJ15003 power transistor

- Power Transistor: $P = 25 \text{ W}$; $\Theta_{jc} = 0.7 \text{ }^{\circ}\text{C/W}$
- Assume $\Theta_{ca} = 5 \text{ }^{\circ}\text{C/W}$
- Ambient Temperature $T_a = 50 \text{ }^{\circ}\text{C}$
- Max. Junction Temperature: $150 \text{ }^{\circ}\text{C}$
- Bepaal Junction-temperatuur zonder heatsink
- Welke heatsink is nodig?
 - Mica-washer: $\Theta = 0.5 \text{ }^{\circ}\text{C/W}$


Oplossing:

- $\Delta T_{ja} = T_j - T_a = 25 \times (0.7 + 5) = 142.5 \text{ }^{\circ}\text{C}$
 - $T_a = 50 \text{ }^{\circ}\text{C} \Rightarrow T_s = 192.5 \text{ }^{\circ}\text{C}$
- $\Delta T_{ja} = T_j - T_a = 25 \times (0.7 + 0.5 + \Theta_H)$
 - $150 - 50 = 30 + 25 \cdot \Theta_H$
 - $\Theta_H = 70/25 = 2.8 \text{ }^{\circ}\text{C/W}$


Classes of Amplifiers

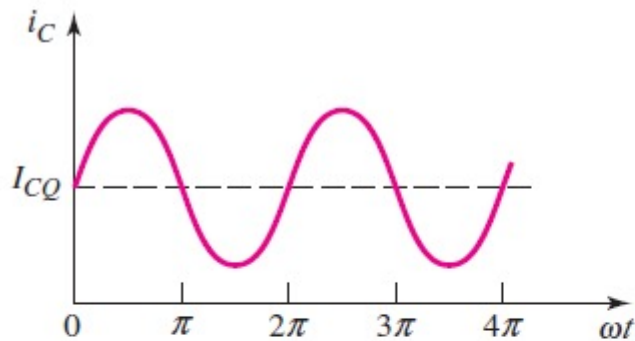


(a)

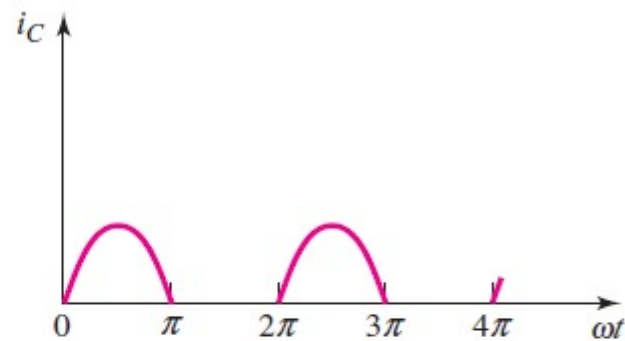

(b)

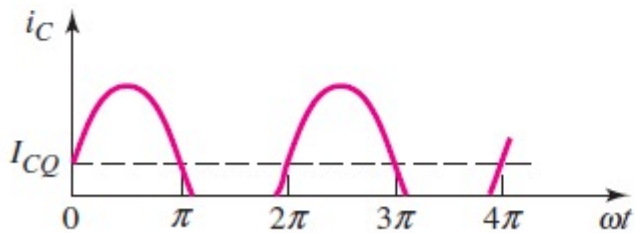

(c)

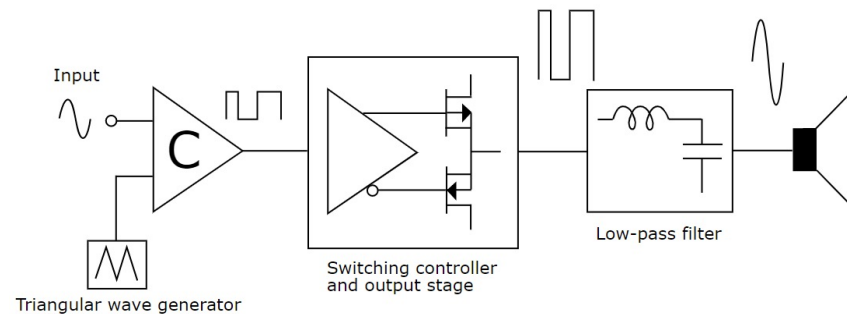

(a) Class A

(c) Class AB

(b) Class B

(d) Class D


Class A amplifier

Advantage:

- Lowest distortion => high-quality amplifier

Disadvantage:

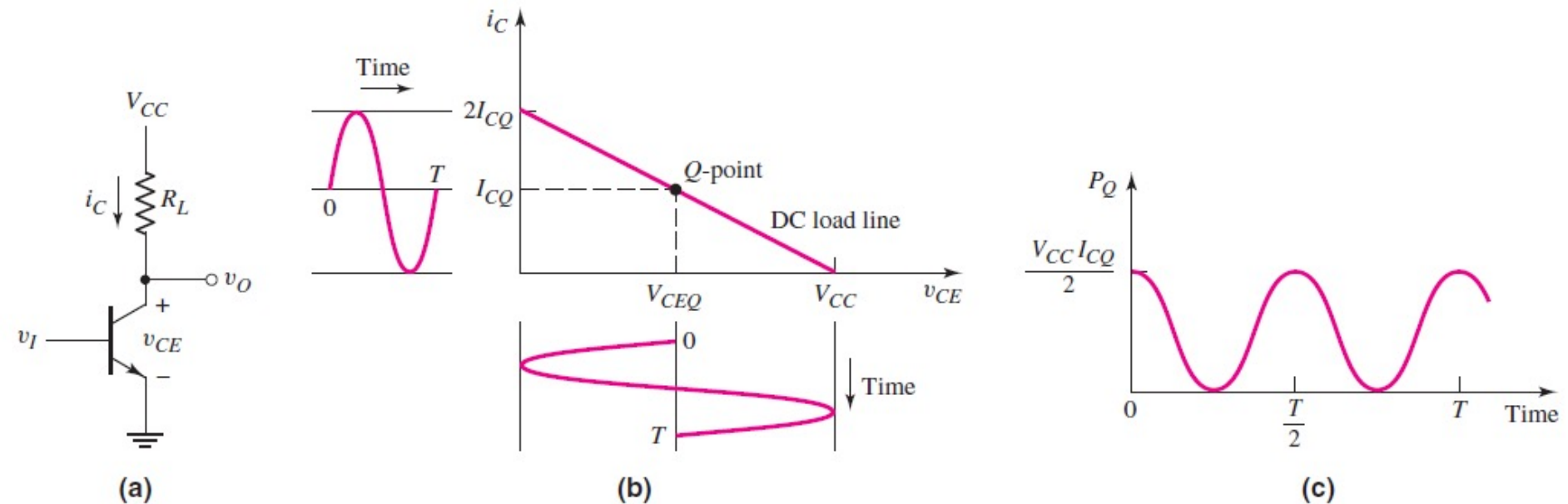- Always on => low-efficiency (10-15 % max.)
- Large heatsinks



Class B amplifier

- Class B not a practical amplifier
 - Because of BJT imperfections
 - Crossover distortion as a result

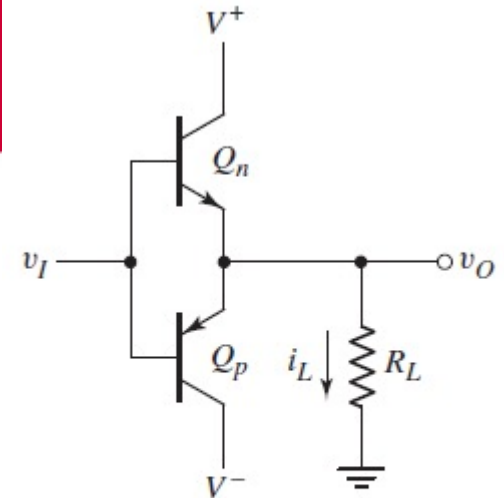


Figure 8.19 Basic complementary push-pull output stage

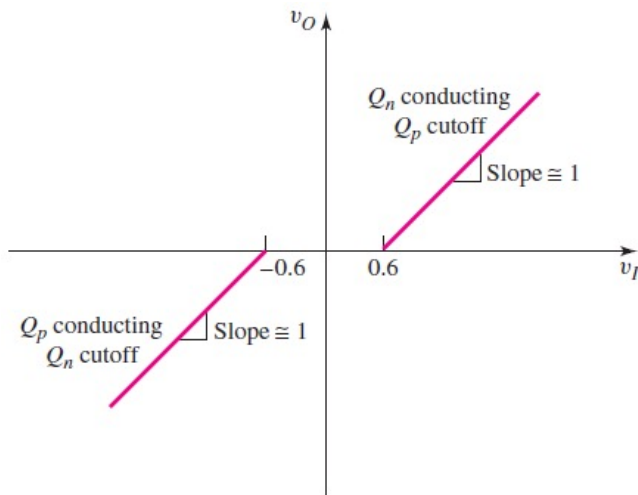


Figure 8.20 Voltage transfer characteristics of basic complementary push-pull output stage

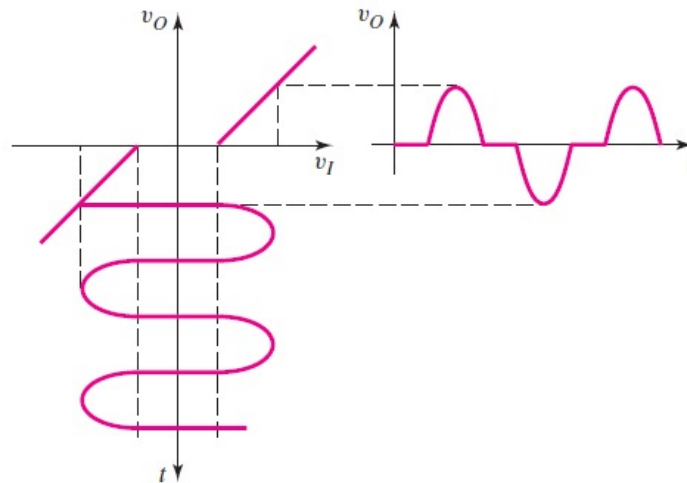


Figure 8.21 Crossover distortion of basic complementary push-pull output stage

Class AB amplifier

Difference with Class B:

- Small bias current set
- Most practical amplifiers use this
- V_{be} multiplier (bias voltage) needed

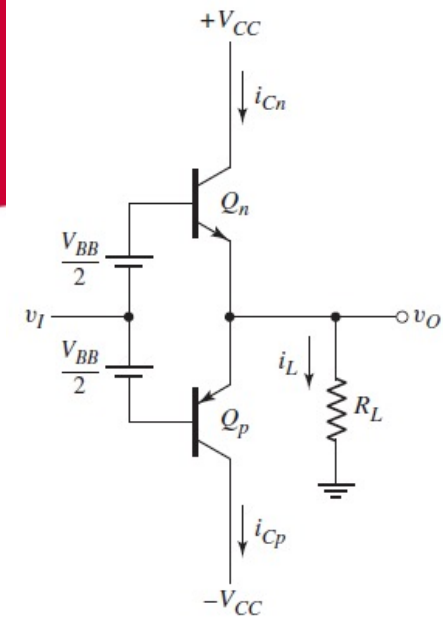


Figure 8.24 Bipolar class-AB output stage

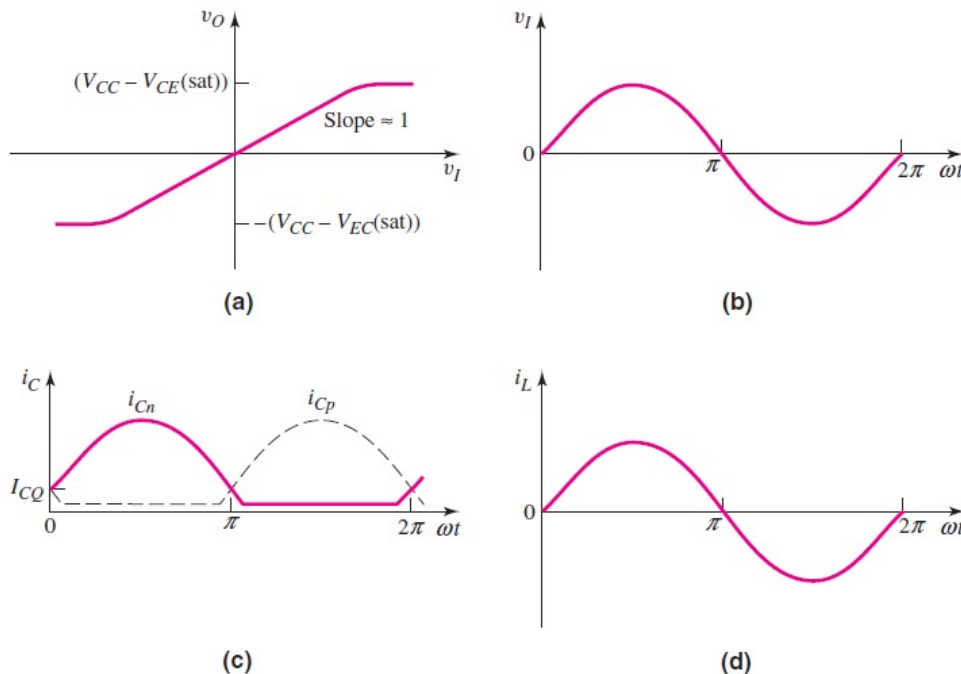


Figure 8.25 Characteristics of a class-AB output stage: (a) voltage transfer curve, (b) sinusoidal input signal, (c) collector currents, and (d) output current


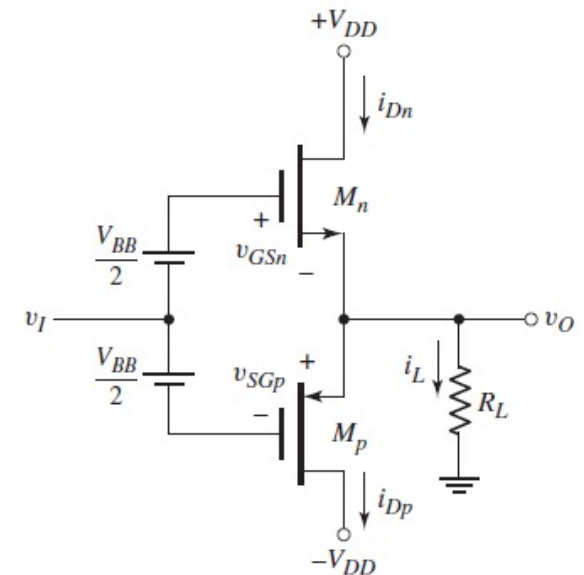


Figure 8.26 MOSFET class-AB output stage

Class D amplifier

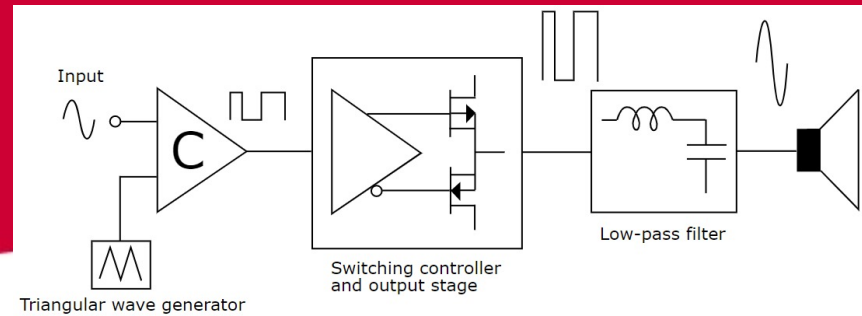

Typical for a Class D amplifier

- Input converted to bitstream
- Bitstream switches MOSFETs push-pull stage
- High switching-frequency needed

Typical components used:

- ADC / sigma-delta converter
- Gate driver with bootstrap voltage
- MOSFET push-pull stage
- LC-filter to remove switching-frequency




500 W IRS2092

Class D amplifier

AD-conversion principle in our Class D-amplifier:

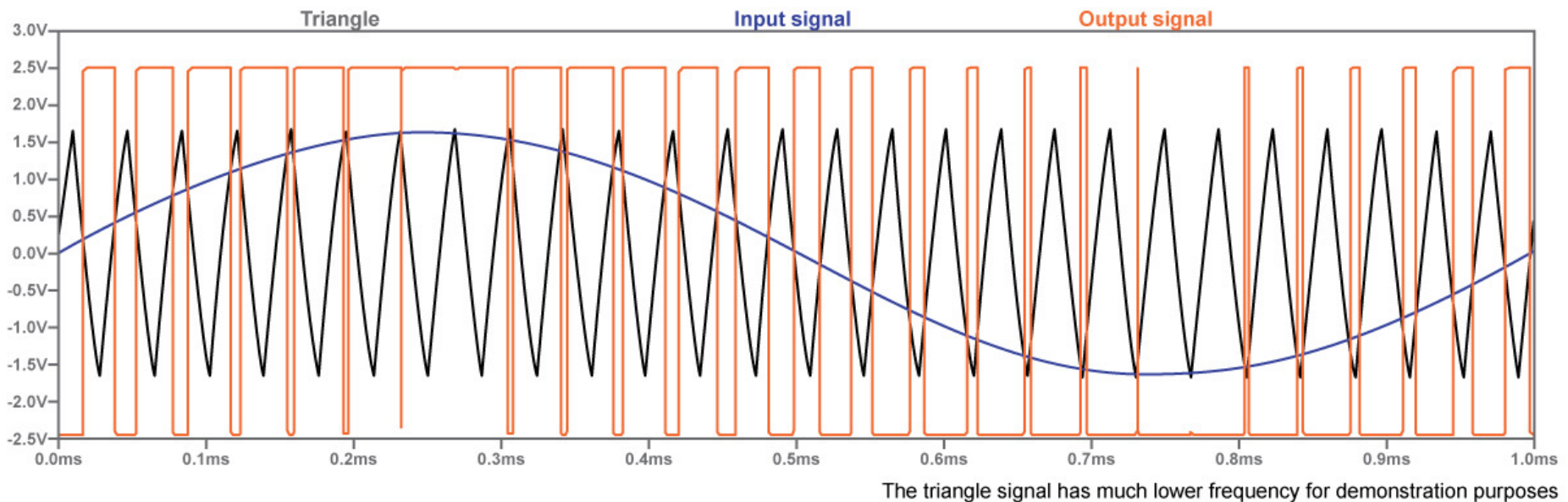■ Input signal compared with triangle-waveform signal



Components used

LM393:

- Dual Comparator
- Open-Collector output


IR2110:

- High and Low side Driver
- Bootstrap voltage

IRF540N:

- N-channel Power MOSFET
- $R_{DS(on)} = 77 \text{ m Ohm}$
- $R_{th,JC} = 1.0 \text{ C/W}$
- $R_{th,CS} = 0.5 \text{ C/W}$
- Non-isolated: Case = Drain !!

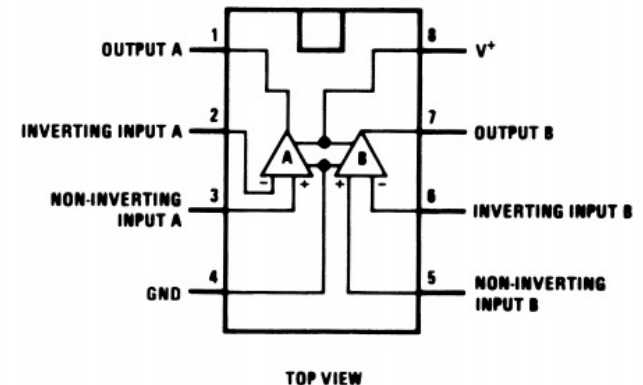P and D Package
8-Pin CDIP, PDIP, SOIC
Top View



$$P_{\text{audio}} = 100 \text{ W}_{\text{rms}}$$
$$R_{\text{speaker}} = 4 \text{ Ohm}$$

$$I_{\text{peak}} = ? \text{ A}$$

$$P_{\text{IRF540}} = ? \text{ W}$$

Transfer function 2nd order LPF

❑ Legend:

- ❑ Q_c : quality factor of the filter, determines ripple in passband
- ❑ ξ : demping factor = $1/(2.Q_c)$
- ❑ ω_c : the cut-off frequency of the filter (in rad/sec.)
- ❑ k : filter gain

❑ Note

- ❑ Numerator does not contain terms with s!

$$H(s) = \frac{k.\omega_c^2}{s^2 + \frac{\omega_c}{Q_c}.s + \omega_c^2}$$

Example (from AFD Toolbox)


□ Butterworth, $f_c=100$ Hz, order $N=2$

□ $Q_c = \frac{1}{2} \cdot \sqrt{2}$

□ $\omega_c = 200 \cdot \pi$

□ $k = 1$
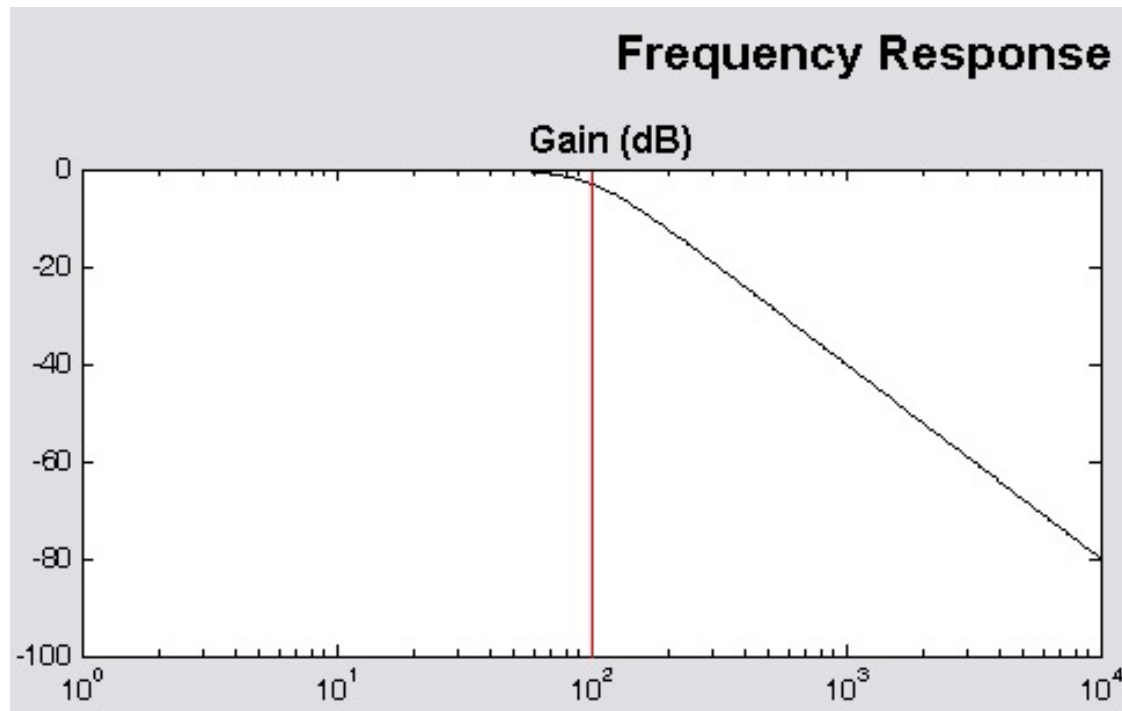
$$H(s) = \frac{a_0}{s^2 + b_1 s + b_0} = \frac{394784}{s^2 + 888,577 s + 394784}$$




MATLAB:

```
f=100; k = 1  
wc=2*pi*f  
Qc=1/sqrt(2)  
b = [0 0 k*wc^2]  
a = [1 wc/Qc wc^2]  
bode(tf(b,a))
```

Quality factor Q_c

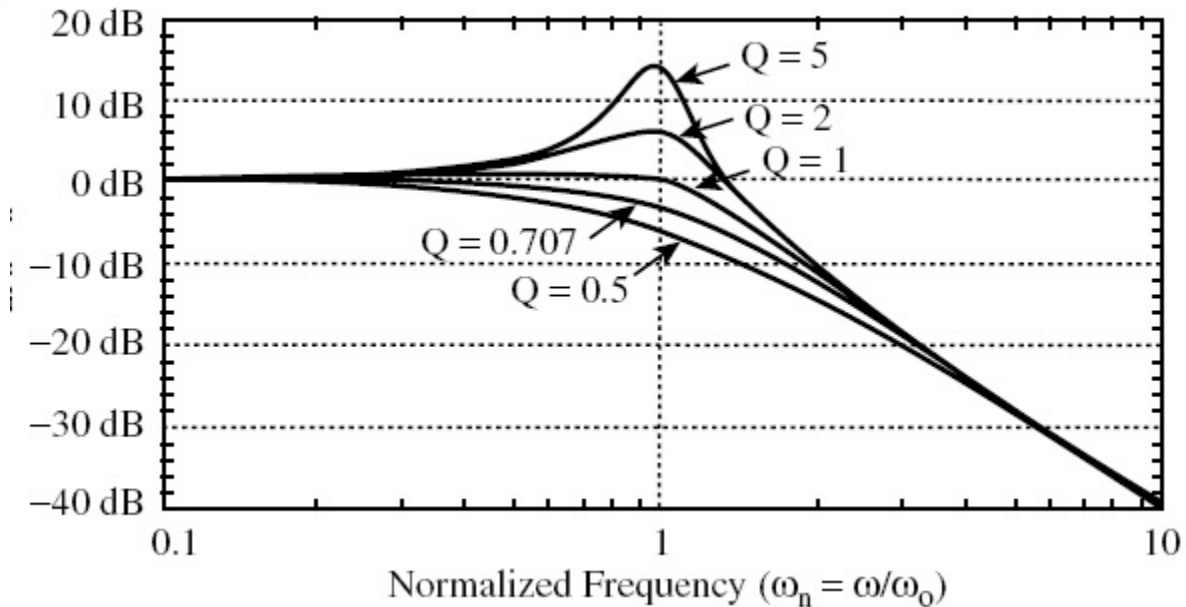□ Quality factor Q_c vs frequency response:



□ Peak:

□ $Q_c = 1/2$: -6 dB

□ $Q_c = 1/2 \cdot \sqrt{2}$: -3 dB

□ $Q_c = 1$: +1.25 dB

□ $Q_c = 2$: +6.3 dB

$$Piek(dB) = 20 \cdot \log \left(\frac{Q_c}{\sqrt{1 - \frac{1}{4Q_c^2}}} \right)$$

(R)LC filter in the Class D amplifier

- $R = R_L = \text{speaker } (4 \Omega)$
- C parallel with R gives ($s = j\omega$):


$$Z_{C//R} = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{1+j\omega RC} = \frac{R}{1+sRC}$$

- $H(s) = \frac{V_O}{V_I} = \frac{\frac{R}{1+sRC}}{\frac{R}{1+sRC} + sL} = \frac{R}{R+sL+s^2LRC}$

- $H(s) = \frac{\frac{1}{LC}}{\frac{1}{LC} + \frac{s}{RC} + s^2}$

- $\omega_c = \frac{1}{\sqrt{LC}}$

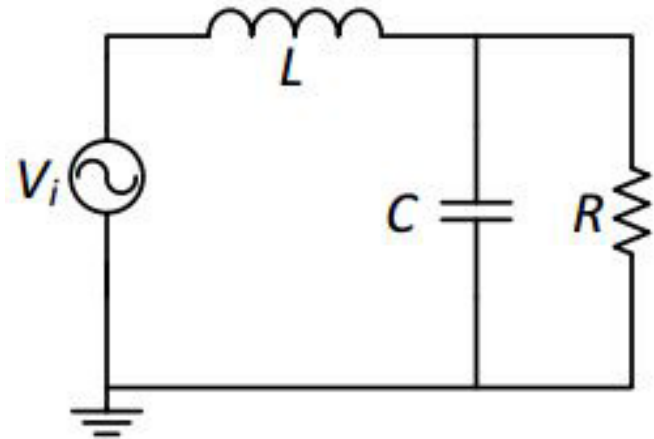
- $\frac{\omega_c}{Q_c} = \frac{1}{RC} \Rightarrow Q_c = R \cdot \sqrt{\frac{C}{L}}$






$$H(s) = \frac{k \cdot \omega_c^2}{s^2 + \frac{\omega_c}{Q_c} \cdot s + \omega_c^2}$$

Bootstrap Design

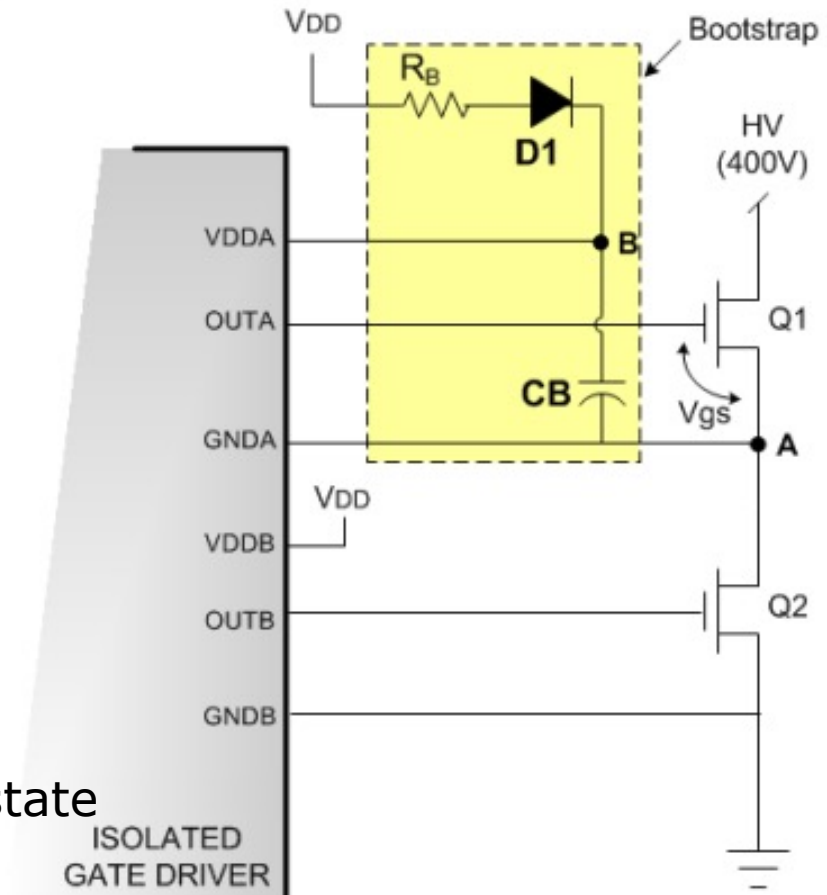- Mosfet half-bridge
 - High-side and low-side mosfets
 - V_{gs} voltage determines on/off state
 - Q_1 source jumps to HV when on
 - Q_1 gate voltage should be higher!
- Mosfet gate:
 - Basically a capacitor
 - Charge Q_G needed for on-state
 - Charge should be removed for off-state




Bootstrap Circuit

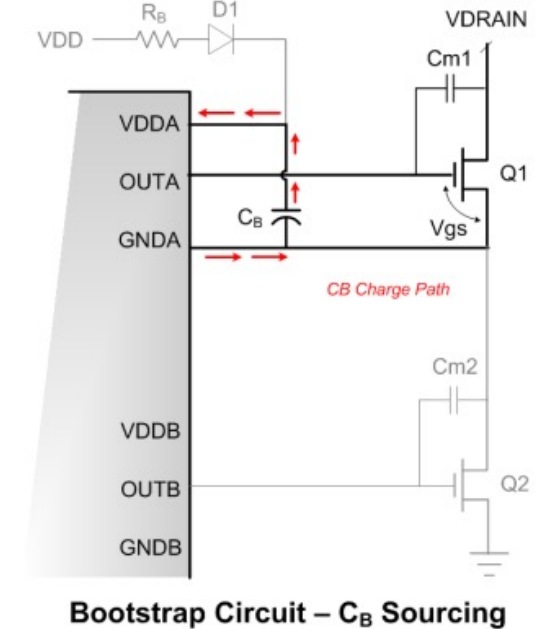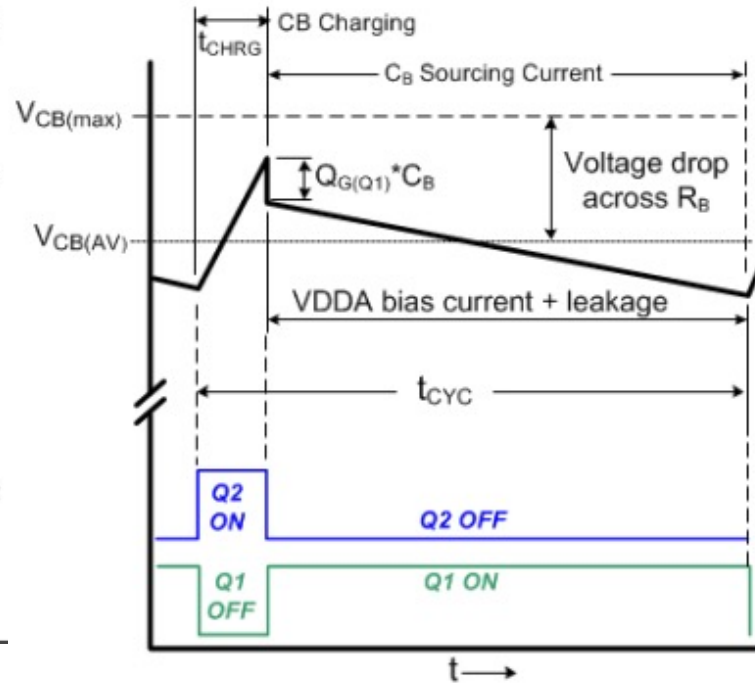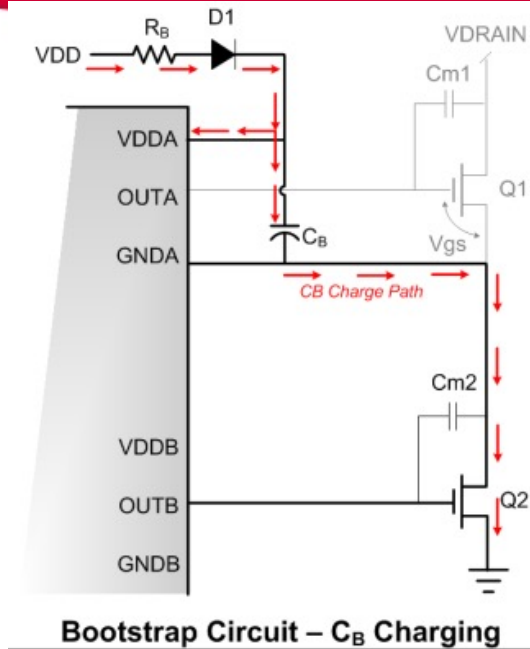


- Q_2 on
 - C_B is charged up to V_B Volts

- Q_1 on
 - C_B sources OUTA/ Q_1

Bootstrap Equivalent Circuit

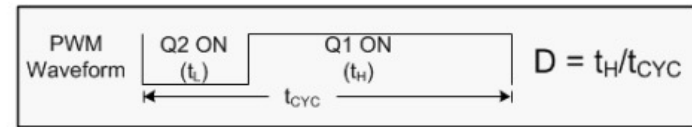

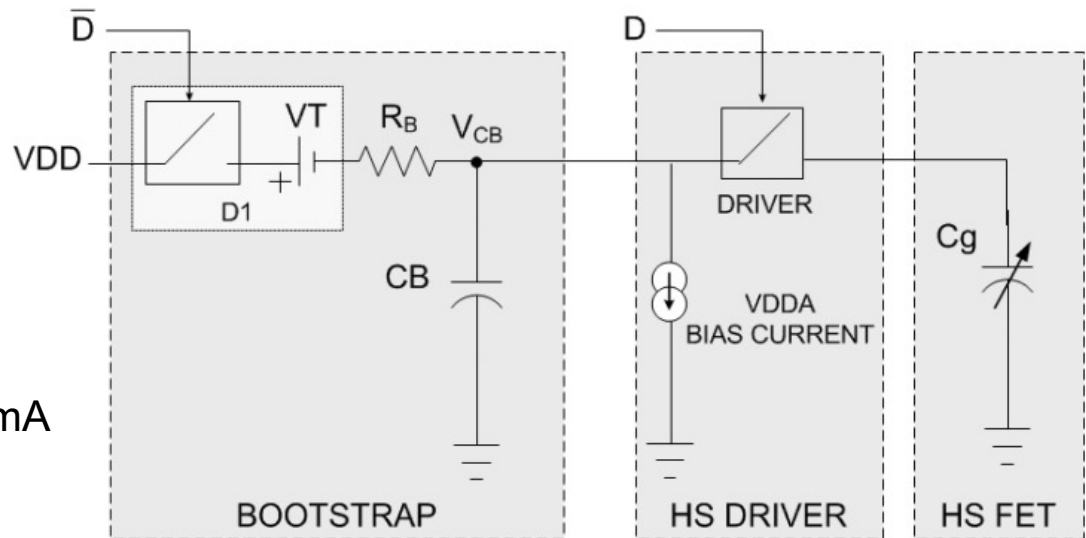- IRF540N
 - $Q_G = 94 \text{ nC}$
- IR2110 gate-driver
 - V_{BS} supply-current = $230 \mu\text{A}$
- Class D design:
 - $I_{Rgs} = (12-0.7) \text{ V}/1 \text{ k}\Omega = 11.3 \text{ mA}$
 - $f_{cyc} = 200 \text{ kHz} \Rightarrow T_{cyc} = 5 \mu\text{s}$
 - D between 10% and 90 %
 - V_{in} between -1.5 V and $+1.5 \text{ V}$



- Total charge Q_{CB} :
 - To be delivered by C_B during max. duty-cycle (90 %)

$$Q_{CB} = Q_G + D \cdot t_{cyc} \cdot (230 \mu\text{A} + 11.3 \text{ mA})$$

$$Q_{CB} = 94 \text{ nC} + 0.9 \cdot 5 \mu\text{s} \cdot 11.53 \text{ mA} = 146 \text{ nC}$$

Bootstrap Equivalent Circuit: C_B calculation

- Total charge Q_{CB} :

- To be delivered by C_B during max. duty-cycle (90 %)

$$Q_{CB} = Q_G + D \cdot t_{cyc} \cdot (230 \mu A + 11.3 \text{ mA})$$

$$Q_{CB} = 94 \text{ nC} + 0.9 \cdot 5 \mu s \cdot 11.53 \text{ mA} = 146 \text{ nC}$$

- Max. allowable ripple (ΔV_{CB}) set to 5 % of V_{DD}

- IR2110 undervoltage threshold = 9.4 V

- C_B calculation:

$$C_B \geq \frac{Q_{CB}}{\Delta V_{CB}} = \frac{146 \text{ nC}}{0.6 \text{ V}} = 243 \text{ nF}$$

- Use 330 nF to be safe

- R_B calculation:

$$5 \cdot R_B \cdot C_B \leq (1 - D_{MAX}) \cdot t_{CYC}$$

$$R_B \leq \frac{0.1 \cdot 5 \mu s}{5 \cdot 330 \text{ nF}} = 300 \text{ m}\Omega$$

- Eliminated from design
 - Only needed for low-frequency applications

Coil calculations

- Magnetic flux in a coil:

- $\Theta = B \cdot A$
- B = flux density, with $B = \mu \cdot H = \frac{\mu \cdot N \cdot I}{l}$
- A = area of coil, l = length of coil (in datasheet: **A_E** and **L_E**)
- $\mu = \mu_0 \cdot \mu_R$, met $\mu_0 = 4\pi \cdot 10^{-7}$ H/m


- Inductance of a coil:

$$L = \frac{N \cdot \Theta}{I} = \frac{N \cdot B \cdot A_E}{I} = N \cdot \frac{\mu \cdot N \cdot I}{l_E \cdot I} \cdot A_E = \mu \cdot \frac{N^2 \cdot A_E}{l_E}$$

Part Number:

T106-2

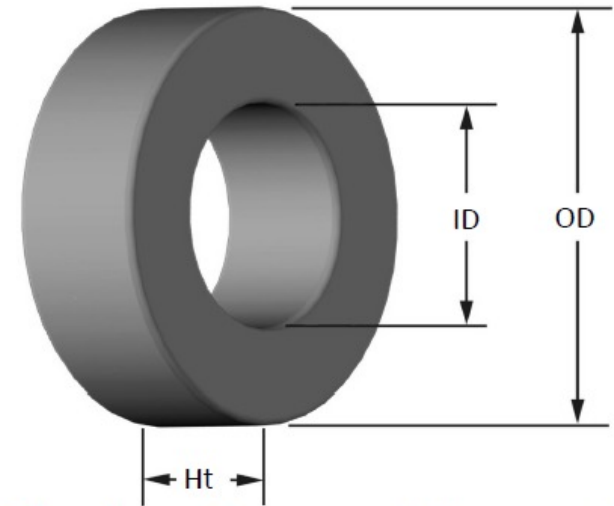Revision 20190524 - Generated 2019-May-30



OD	(nom. - bare core)	26.92 mm	1.060 in
	(max. - after coating)	27.43 mm	1.080 in
ID	(nom. - bare core)	14.48 mm	0.570 in
	(min. - after coating)	13.97 mm	0.550 in
Ht	(nom. - bare core)	11.10 mm	0.437 in
	(max. - after coating)	11.73 mm	0.462 in
Mass	(approximate)	21 grams	
Magnetic Dimensions	A _e - Eff. Mag. Cross Section	0.659 cm ²	
	L _e - Eff. Mag. Path Length	6.49 cm	
	V _e - Eff. Core Volume	4.28 cm ³	
	WA - Min. Eff. Window Area	1.53 cm ²	
	sa - Surface Area	28.1 cm ²	
	mlt - mean length per turn	4.39 cm	
	μ _i (reference)	10	

Class D amplifiers